

Student ID: _____

ICS 151 Quiz 5

Name : _____ , _____
(Last Name) (First Name)

Student ID : _____

Signature : _____

Instructions:

1. Please verify that your paper contains **4 pages** including this cover.
2. Write down your Student-Id on the top of each page of this quiz.
3. This exam is **closed book**. No notes or other materials are permitted.
4. Total credits of this quiz are **50 points**.
5. To receive credit you must show your work clearly.
6. **No re-grades will be entertained if you use a pencil.**
7. Calculators are **NOT** allowed.

Student ID: _____

Q1: Function Minimization

[30 points]

Consider function F with the following equation:

$$F(a,b,c,d) = a'b'c'd' + a'bc'd' + a'bc'd + abcd + abcd' + ab'cd' + ab'c'd'$$

Assuming that $abcd = 0011$ never happens in the input (so you can regard it as don't care situation):

a. Fill the following K-map table (5 points)

	cd	00	01	11	10
ab					
00		1 m ₀	0 m ₁	X m ₃	0 m ₂
01		1 m ₄	1 m ₅	0 m ₇	0 m ₆
11		0 m ₁₂	0 m ₁₃	1 m ₁₅	1 m ₁₄
10		1 m ₈	0 m ₉	0 m ₁₁	1 m ₁₀

b. Identify Prime Implicants and Essential Prime Implicants. (15 points)**Prime Implicants:**

$$m_4 + m_5 = a'bc'$$

$$m_0 + m_4 = a'c'd'$$

$$m_0 + m_8 = b'c'd'$$

$$m_8 + m_{10} = ab'd'$$

$$m_{10} + m_{14} = acd'$$

$$m_{14} + m_{15} = abc$$

Essential Prime Implicants:

$$m_4 + m_5 = a'bc'$$

$$m_{14} + m_{15} = abc$$

c. Using the K-map table in 1(a), write the minimized equation for function F. (10 points)

Minimized equation = Essential Prime Implicants, +
non-Essential Prime Implicants

$$= [(m_4 + m_5) + (m_{14} + m_{15})] +$$

$$[(m_4 + m_0) + (m_8 + m_{10})]$$

$$= a'bc' + abc + a'c'd' + ab'd'$$

Student ID: _____

Q2: Size-Delay trade off

[20 points]

Show the trade-off in delay vs. size for the circuit representing function F.

$$F(a,b,c,d,e,f) = abcd + cdef + abc$$

You can use the following gate library showing costs for different gates:

Gate	Cost
2-input AND	4
3-input AND	6
2-input OR	4
3-input OR	6

