

Student ID: \_\_\_\_\_

# CS 151 Quiz 3

Name : \_\_\_\_\_ , \_\_\_\_\_  
(Last Name) (First Name)

Student ID : \_\_\_\_\_

Signature : \_\_\_\_\_

## **Instructions:**

1. Please verify that your paper contains **8 pages** including this cover.
2. Write down your Student-Id on the top of each page of this quiz.
3. This exam is **closed book**. No notes or other materials are permitted.
4. Total credits of this quiz are **45 points**.
5. To receive credit you must show your work clearly.
6. **No re-grades will be entertained if you use a pencil.**
7. Calculators are **NOT** allowed.


Student ID: \_\_\_\_\_

**Q1: [Controller Design]**

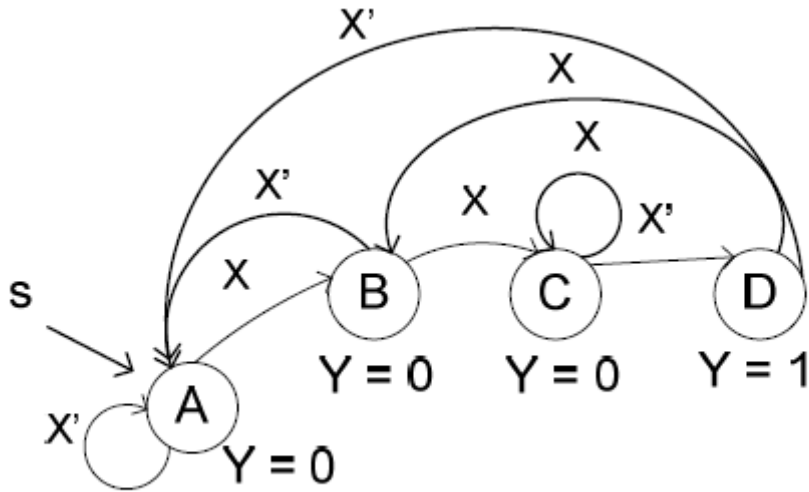**[15 points]**

Considering the FSM shown below:

X is the input to the FSM and Y is the output associated with each state.



a) Create the architecture for this FSM. [5 points]

Student ID: \_\_\_\_\_

**b)** Considering the state encoding shown below, draw the state table. **[10 points]**

A = 00, B = 01, C = 10, D = 11

NOTE: Just write the equation for the output Y.

Student ID: \_\_\_\_\_

**Q2: [FSM Design]**

**[10 points]**

Design an FSM which detects strings of the form of  $1(01)^*$  on the stream of input X. On the detection of the string, an output Y should become 1.

$1(01)^*$  are a class of strings that start from 1, followed by any number of 01 (at least 0).

NOTE: 1, 101, 101...01, etc are some samples of a string of form  $1(01)^*$ .

Student ID: \_\_\_\_\_

<This page is intentionally left blank>

Student ID: \_\_\_\_\_

**Q3: [Registers]**

**[20 points]**


Design inside the Black Box below to implement a 4-bit register with the functionality specified in the following table. ( $A = a_3a_2a_1a_0$  is the output of the register.)

$B = b_3b_2b_1b_0$  is the input to the register.

NOTE: Specify the select lines of each multiplexer as well as the inputs. You can use the following components if needed.

- Adder
- Comparator
- Logic gates

$S_1S_0$	Action	Output
00	Load	$b_3b_2b_1b_0$
01	Keep current value	A
10	If $(B > A) \rightarrow$ Load B; else Keep current value	If $(B > A) \rightarrow B$ ; else A;
11	If $(B > 2 * A) \rightarrow$ Load $B/2$ ; else Load $A/2$	If $(B > 2 * A) \rightarrow B/2$ ; else $A/2$ ;

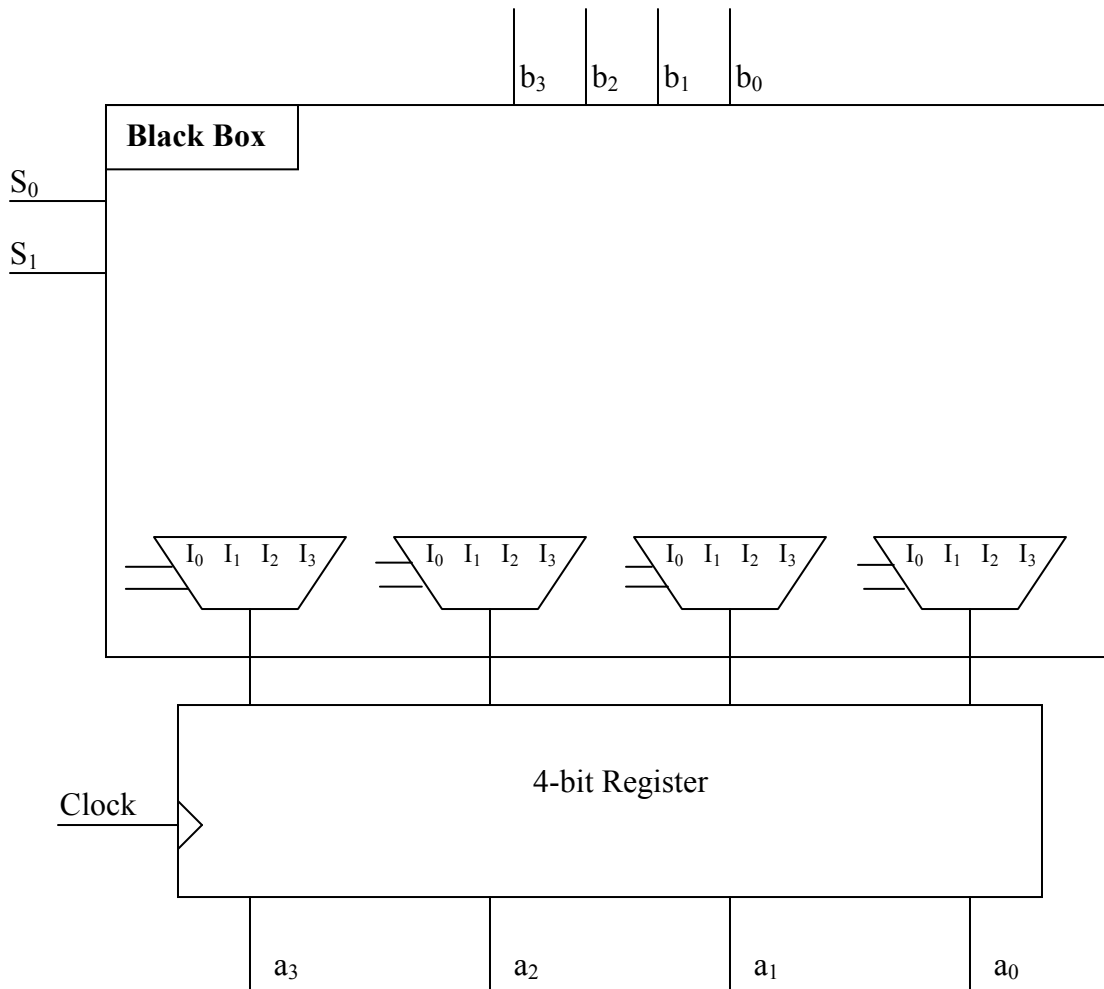

Student ID: \_\_\_\_\_

<This page is intentionally left blank>

Student ID: \_\_\_\_\_

<This page is intentionally left blank>