

Student ID: _____

CS 151 Quiz 5

Name : _____ , _____
(Last Name) (First Name)

Student ID : _____

Signature : _____

Instructions:

1. Please verify that your paper contains **7 pages** including this cover.
2. Write down your Student-Id on the top of each page of this quiz.
3. This exam is **closed book**. No notes or other materials are permitted.
4. Total credits of this quiz are **45 points**.
5. To receive credit and for possible re-grade request you must show your work clearly.
6. **For possible re-grade request make sure that your write clearly.**
7. Calculators are **NOT** allowed.

Student ID: _____

Question 1 |State minimization|

[15 points]

- a. Reduce the number of states in the following state table using the implication table method. **(10 points)**

Present state	Next State		Output
	X=0	X=1	
A	F	C	0
B	C	E	1
C	A	E	1
D	A	C	0
E	B	G	0
F	D	C	0
G	B	C	1

Notice that this state table is for a **Moore** machine.

A = D = F

<u>A</u>							
<u>B</u>	X						
<u>C</u>	X	(A,C) (E,E)					
<u>D</u>	(A,F) (C,C)	X	X				
<u>E</u>	(B,F) (G,C)	X	X	(C,A) (G,C)			
<u>F</u>	(D,F) (C,C)	X	X	(D,A) (C,C)	(D,B) (C,G)		
<u>G</u>	X	(F,C) (C,E)	(F,A) (C,E)	X	X	X	
	<u>A</u>	<u>B</u>	<u>C</u>	<u>D</u>	<u>E</u>	<u>F</u>	<u>G</u>

Student ID: _____

b. Tabulate the reduced state table using the table provided below. (5 points)

Present state	Next State		Output
	X=0	X=1	
ADF	ADF	C	0
B	C	E	1
C	ADF	E	1
E	B	G	0
G	B	C	1

Student ID: _____

Question 2 [Function Minimization]

[20 points]

Consider function F with the following equation:

$$F(a,b,c,d) = ac'd' + abcd' + bc'd + a'b'cd'$$

Assuming that $abcd = 0000$ and $abcd = 1010$ never happen in the input (so you can regard them as don't care situations),

1. Fill the following K-map table (5 points)

	cd				
ab		X	0	0	1
		m ₀	m ₁	m ₃	m ₂
		0	1	0	0
		m ₄	m ₅	m ₇	m ₆
		1	1	0	1
		m ₁₂	m ₁₃	m ₁₅	m ₁₄
		1	0	0	X
		m ₈	m ₉	m ₁₁	m ₁₀

Student ID: _____

2. Identify Prime Implicants and Essential Prime Implicants. (10 points)

Prime Implicants:

$$m_0 + m_2 + m_8 + m_{10} = b'd'$$

$$m_8 + m_{12} = ac'd' \quad , \quad m_{12} + m_{13} = abc' \quad , \quad m_5 + m_{13} = bc'd$$

$$m_{12} + m_{14} = abd'$$

Essential Prime Implicants:

$$m_0 + m_2 + m_8 + m_{10} = b'd'$$

$$m_5 + m_{13} = bc'd$$

$$m_{12} + m_{14} = abd'$$

3. Using the K-map table in 1(a), write the minimized equation for function F. (5 points)


$$F = b'd' + bc'd + abd'$$

Student ID: _____

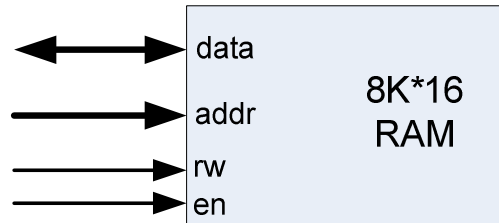Question 3 [Memory Design]

[10 points]

Design a 32K*32-bit RAM using 8K*16-bit RAM modules shown below.



8K*16-bit RAM Module

Use a minimum number of the following logic components in your design (*no other components may be used for this design*):

- 1) Priority Encoder
- 2) Decoder
- 3) Multiplexer

NOTE: All the 8K*16 modules share the same line for rw, so that input is not shown in the solution.

Student ID: _____

<This page is intentionally left blank>

