

Student ID: _____

ICS 151 Midterm

Name : _____ , _____
(Last Name) (First Name)

Student ID : _____

Signature : _____

Instructions:

1. Please verify that your paper contains **5 pages** including this cover.
2. Write down your Student-Id on the top of each page of this quiz.
3. This exam is **closed book**. No notes or other materials are permitted.
4. Total credits of this midterm are **30 points**.
5. To receive credit you must show your work clearly.
6. **No re-grades will be entertained if you use a pencil.**
7. Calculators are **NOT** allowed.

Solution

Student ID: _____

Q1: Circuit Design


[20 points]

We want to design a **frequency divider** circuit that divides a given frequency by 3 or 5. If the input **MODE=0** it divides the frequency by 3 and if **MODE= 1** it divides the frequency by 5. Use as many of the following as needed in your design:

- a- 3-bit counter with clear
- b- 2-to-1 multiplexer
- c- Logic gates (AND, OR, NOT)

Hint: Use mod-3 and mod-5 counters.

First Method

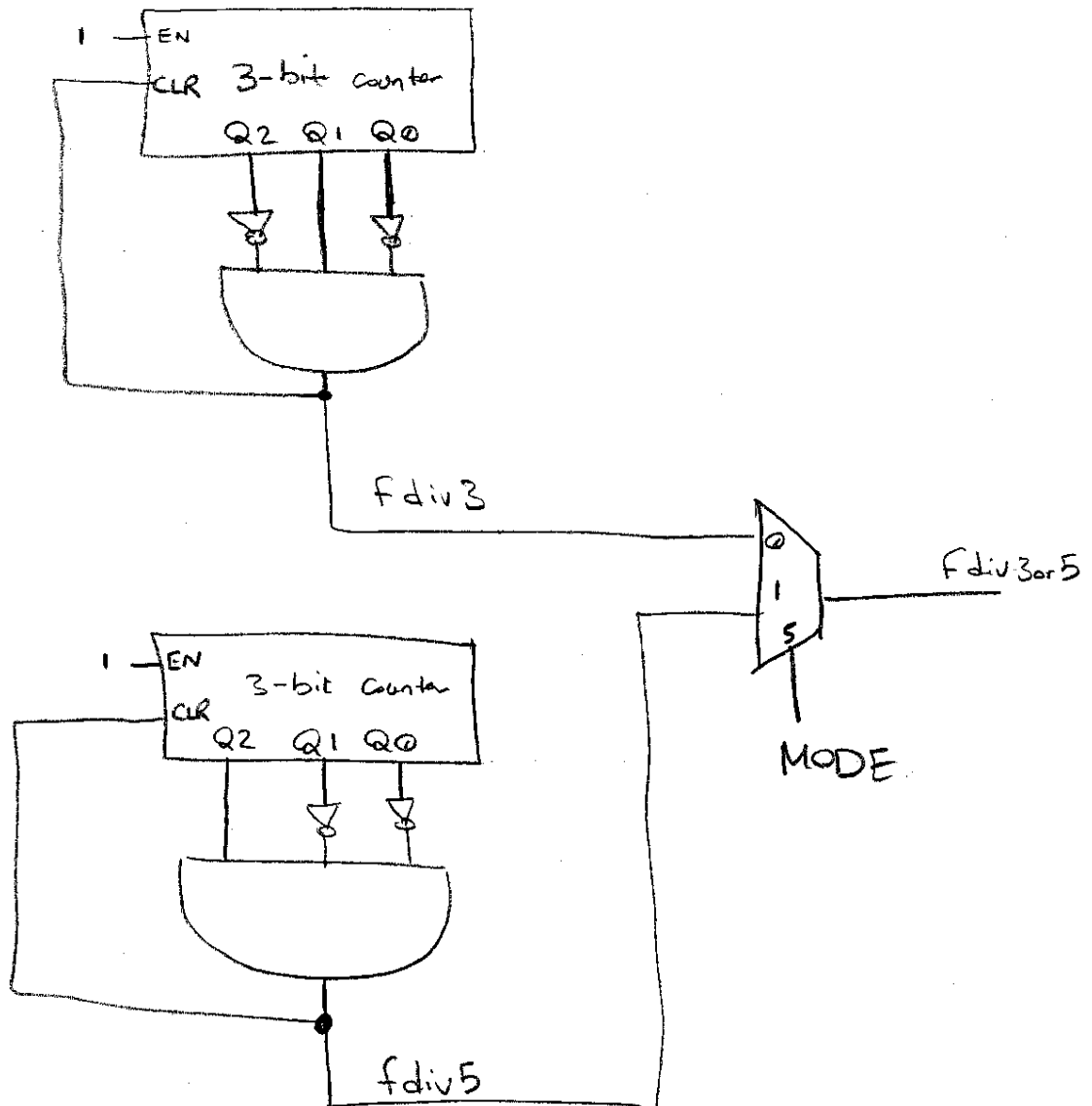


Student ID: _____

This page is blank intentionally

Second Method

$$x \oplus 0 = x$$

$$x \oplus 1 = \overline{x}$$

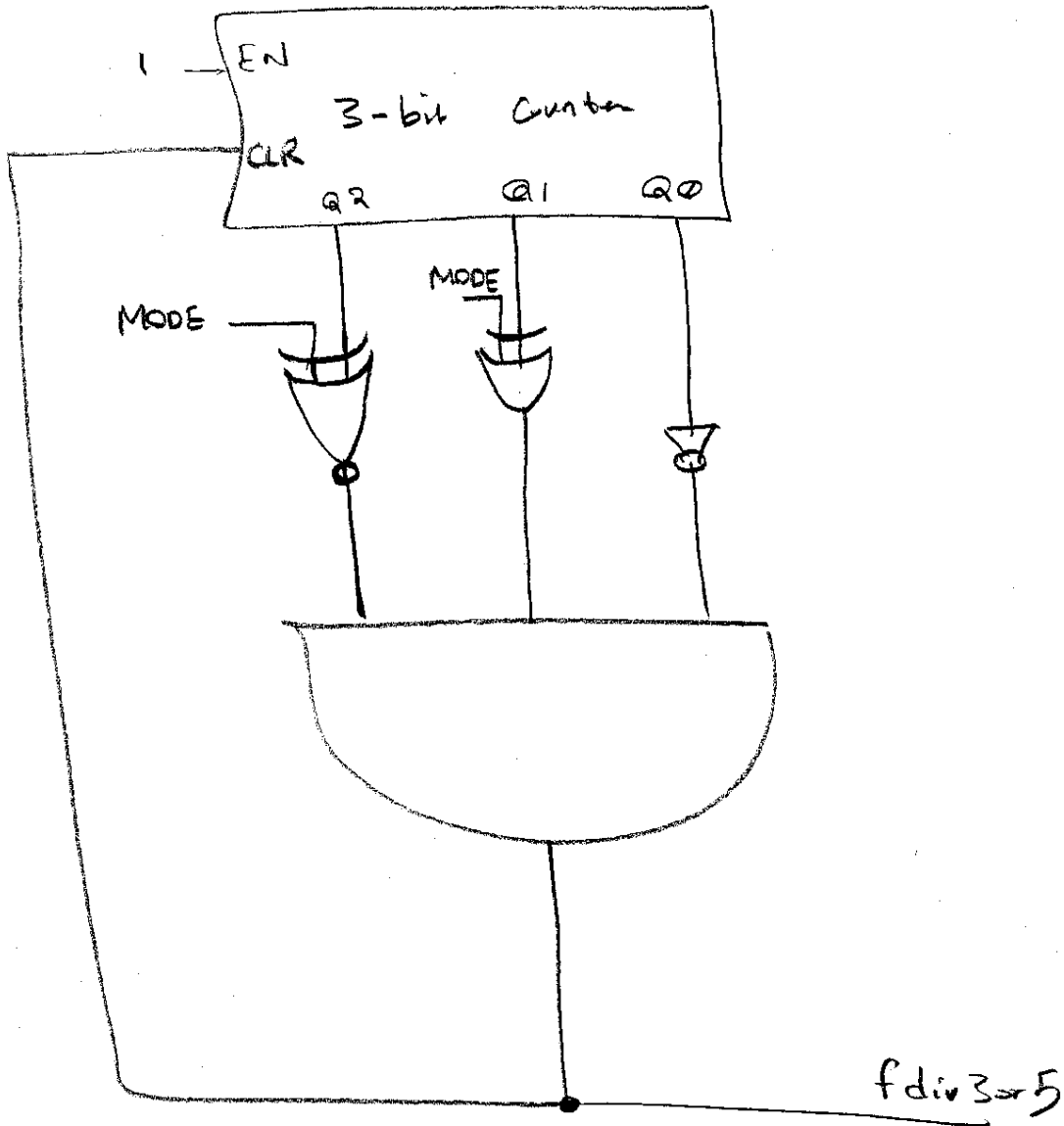

Student ID: _____

Q2: Overflow detector for 2's complement [10 points]

We want to add two n-bit 2's complement numbers A and B which has the following forms:

$$A = a_{n-1}a_{n-2}\dots a_0$$

$$B = b_{n-1}b_{n-2}\dots b_0$$

Let's call the carry out of the (n-2)nd stage, c_{n-1} ; the carry out of the the (n-1)st stage, c_n and (n-1)st bit of sum as s_{n-1} .

a - Complete the following table ('Overflow' output shows that overflow happened):

Input			Output		
a_{n-1}	b_{n-1}	c_{n-1}	c_n	s_{n-1}	Overflow
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

b- Express the Overflow condition in term of c_n and c_{n-1} only. (Note that this is another method for deriving the 2's complement overflow condition).

$$\begin{aligned} \text{Overflow} &= c_{n-1} \cdot \overline{c_n} + \overline{c_{n-1}} \cdot c_n \\ &= c_{n-1} \oplus c_n \end{aligned}$$