

Solutions for Homework 4

5. Use the table from hw2-1, #1a:

A	B	C	E
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

The inputs d1, d2, d4, and d7 of the multiplexer in Fig. 3-12a are set to 1, the rest is set to 0. (Analogous to Fig. 3-12b.)


- 8.

A0	A1	B0	B1	E
0	0	0	0	1
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	1
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	1
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	1

$$E = A0'A1'B0'B1' + A0'A1B0'B1 + A0'A1B0'B1 + A0A1B0B1$$

The diagram has 4 AND gates (with 4 inputs each); the four AND gates are connected to an OR gate. (Analogous to circuit Fig 3-3b, only with 4 inputs A0, A1, B0, B1, instead of A, B, C.)

10.

 


11. Simply connect a 1 to the one input of the demultiplexer. The 3 control lines ABC are then “decoded” onto the 8 output lines d_0 - d_7 . I.e., when $ABC=000$, $d_0=1$, when $ABC=001$, $d_1=1$, etc.

12. The mux has 4 inputs d_0 - d_3 and 2 controls AB, and output.

- OR gate: connect a 1 to d_1 , d_2 , d_3 . Thus only when $AB=00$ will the output be 0.
- XOR: connect a 1 to d_1 and d_2 .
- NAND: connect a 1 to d_0 , d_1 , d_2 .

13.

 

16.

F0	F1	ENA	ENB	INVA	Cin	Out	Cout
0	0	1	1	0	0	1	0
0	0	0	1	1	1	1	0
1	0	1	1	0	1	0	0
1	0	0	0	0	0	1	0
1	1	1	1	0	1	1	1
1	1	0	1	0	1	0	1
1	1	1	0	1	1	1	0
1	1	0	0	0	1	1	0