

Solutions for Homework 5


19.

t	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
S	0	1	0	1	1	0	0	0	1	1	1	0	0	0	0	0	0	0	1	1	0
R	0	0	0	0	0	0	1	0	0	0	0	0	1	1	0	1	0	0	1	1	0
Q	0	1	1	1	1	1	0	0	1	1	1	1	0	0	0	0	0	0	0	0	?


20.

The design uses two AND gates for chip enable logic plus two AND gates per word select line plus one AND gate per data bit. For a 256×8 memory this comes to $2 + 512 + 2048 = 2562$ AND gates. The circuit also uses one OR gate for each bit in the word; hence eight of them would be needed.

21. a.

 

b.

 

22.

From the midpoint of T1 to the midpoint of T3 it is 40 nsec. So the memory has $40 - T_M - T_{DS} = 40 - 3 - 2 = 35$ nsec to respond.

23.

In regular mode it takes 3 cycles per block, i.e. $3n$ for n blocks. In block mode it takes 3 for the first block and 1 for each subsequent block, i.e., $3+n-1 = 2+n$.

The increase in bandwidth is then $3n/(2+n)$. For large n this approaches 3, i.e., 3 times as much bandwidth using block transfer.