

The Digital Logic Level


- lowest level – just above **transistors**
- digital circuits**
 - collections of **gates** and wires
 - only deal with 0's and 1's
 - described by **Boolean algebra**

Lubomir Bic, UCI

1

Transistors

 - a transistor is a **switch** with
 - one input V_{in}
 - one output V_{out}
 - constant supply voltage V_{cc}
 - a ground



- basic **operation**
 - $V_{cc} = 1$
 - when $V_{in} = 0$, switch is closed $\Rightarrow V_{out} = 1$
 - when $V_{in} = 1$, switch is open $\Rightarrow V_{out} = 0$

- most important observation:
a transistor **inverts** the input signal

V_{in}	V_{out}
0	1
1	0


- transistors are used to implement **gates**

Lubomir Bic, UCI

2

Gates

 - all **digital circuits** are constructed out of gates
- gates** are:
 - the lowest level building blocks
 - described using **Truth Tables**



Lubomir Bic, UCI

3

Boolean Algebra

- truth tables are very cumbersome
- introduce notation to capture only 1's:
 - variables: $A, B, C, \dots$
 - negated variables: A', B', C' (sometimes shown as $\bar{A}$)
 - OR function: $+$
 - AND function: $\cdot$ or just adjacency
- Examples:
 - $A + B = 1$ if $A = 1$ or $B = 1$
 - $AB = 1$ if $A = 1$ and $B = 1$
 - $A' = 1$ if $A = 0$
 - $AB'C = 1$ if ???
- We are now ready to design some basic circuits

Lubomir Bic, UCI

4

A Simple Digital Circuit

- Task: design a circuit to perform **majority** function

- 3 inputs, 1 output
- out = 1 if at least 2 inputs are 1

- Step 1: build a truth table

- M = 1 with majority of ABC

- Step 2: write a Boolean expression

- any truth table is a sum of products
- each row is an AND expression (minterm)
- combined using OR

$$M = A'BC + AB'C + ABC' + ABC$$

A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Lubomir Bic, UCI

5


A Simple Digital Circuit (cont)

$$M = A'BC + AB'C + ABC' + ABC$$

- Step 3: Lay out circuit

- provide inverter for each negated variable
- draw parallel lines for legibility
- provide AND gate for each term
- provide OR gate to combine terms

- not most efficient but it works

 

Lubomir Bic, UCI

6

Circuit Optimization

- main goals

- reduce the total **number** of gates
- use only **one type** of gate (e.g. NAND or NOR)

- for goal 1:

- apply **laws of Boolean algebra** to simplify expression
- then lay out circuit

- for goal 2:

- apply rules of **gate substitution**

Lubomir Bic

7

Laws of Boolean Algebra

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A * BC = (A * B)(A * C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A} \bar{B}$

absorption law

A	B	A+B	A(A+B)
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

- laws 1-6 are intuitive
- distributive law: OR form is intuitive, AND form is the **dual**
- absorption law: consult truth table
- De Morgan: not intuitive but **extremely important**


Lubomir Bic

8


Apply Laws of Boolean Algebra

- Task: implement and simplify function $M = AB + AC$

- as given: need 2 AND gates, 1 OR gate

 

 - apply distributive law: $M = AB + AC = A(B+C)$
- need only 1 OR gate, 1 AND gate



- There are systematic approaches to circuit optimization
 - subject of more advanced courses

Lubomir Bic


9

Gate Substitution


- NOT, AND, OR can be replaced by NAND or NOR only

- NOT A

- using NAND

 


- using NOR

 


- A AND B

- using NAND

 

- using NOR

 


- analogous substitutions exist for A OR B
- How do we know that the substitutions are equivalent?

Lubomir Bic

10

Gate Substitution

 - Task: prove that this is equivalent to (A AND B)



- Approach 1: construct truth table

A	B	X	X	Y
0	0	1	1	0
0	1	1	1	0
1	0	1	1	0
1	1	0	0	1

$$Y = A \text{ AND } B$$

- Approach 2: use laws of Boolean algebra

$$Y = (XX)' = ((AB)' (AB)')' = ((AB+AB)')' = AB+AB = AB$$

from diagram De Morgan double NOT idempotent

Lubomir Bic

11

Gate Substitution


- Let's test our skills:

- design circuit for XOR function using only NAND

- truth table:

- expression: $A \text{ XOR } B = A'B + AB'$

- circuit:

 

A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

- use NAND only:

- replace ANDs with NAND equivalents: 2 for each

- replace OR with NAND equivalent: 3

- resulting circuit: 7 NAND gates!! (no way ...)

- need a better approach

Lubomir Bic


12

Gate Substitution

- De Morgan suggests different substitutions:



 - and **negating both sides** yields yet another set:




- One last insight (trick?):
 - two** inversion bubbles on the same line **cancel** each other
 - $(A')' = A$
- Now we can design with NAND (NOR) only

Lubomir Bic

13

Gate Substitution

 - given an AND/OR/NOT circuit
 - previous example
- place 2 inversion bubbles on each inner line
 - some gates are automatically NAND
- use gate substitutions to get NAND (NOR) only
- works for any canonical circuit:
 - sum of products, product of sums




Lubomir Bic

14

Gate Substitution

 - Practice: implement majority circuit using NAND only



Lubomir Bic

15

Combinational Circuits


- multiple inputs and **multiple** outputs
- output depends **only** on current inputs (no memory)
- general purpose** circuits
 - multiplexers/demultiplexers, encoder/decoders, comparators
- arithmetic** circuits
 - shifters, adders
- used to construct more complex circuits
 - ALUs

Lubomir Bic

16

Multiplexers

 - interface
 - 2ⁿ inputs
 - 1 output
 - n control lines
- basic idea:
 - select one of the inputs D_i to be the output F using ABC
 - 000 selects D₀
 - 001 selects D₁
 - 111 selects D₇
- how does it work?
 - A=0, B=0, C=1
- demultiplexer: connect 1 input to one of 2n outputs




Lubomir Bic

17

Using a Multiplexer

- implement **majority** function using **multiplexor chip**

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

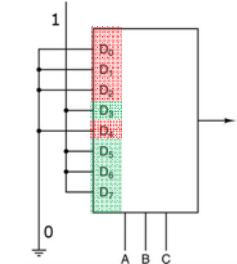

- each line in the table corresponds to one input
 - connect 0 or 1 to inputs based on table
 - ABC chooses the correct output
- Examples: ABC=011, ABC=100

Lubomir Bic

18


Decoders

- interface
 - n inputs
 - 2ⁿ outputs
- basic idea:
 - turn a number into a position

A	B	C	
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	0	0	D4
1	0	1	D5
1	1	0	D6
1	1	1	D7

- how does it do it?

 ABC=000, D₀ needs 111: connect A'B'C'
 ABC=001, D₁ needs 111: connect A'B'C
 ABC=111, D₇ needs 111: connect ABC




Lubomir Bic

19

Comparators

 - interface
 - input: 2 n-bit numbers A, B
 - 1 output
- basic idea:
 - output=1 if A=B
- how does it do it?
 - use XOR gates
 - 1 if A_i or B_i is 1, i.e. **NOT** equal
 - 0 if equal
 - A=B iff **all** lines are 0
 - OR is 0 if all 0's, NOR is 1
- recall how to implement XOR gates (3 NAND or 3 NOR)



Lubomir Bic

20

PLAs


- Programmable Logic Arrays
 - no specific function is predefined
 - superset of all possible canonical functions
 - sum of products
 - chosen function is programmed once – “burnt in”
 - analogous to a CD-R
 - how does it work?
 - every internal variable has both options, X and X'
 - every line has a fuse
 - one of the two fuses is burnt out to chose X or X'

Lubomir Bic

21

PLAs

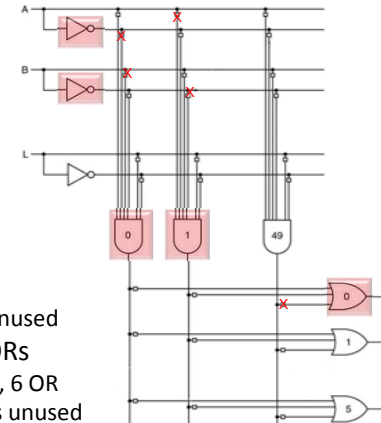
- Example
 - 12 inputs
 - 6 outputs
- implement XOR
 - $F = AB' + A'B$
 - 2 AND, 1 OR, A', B'
 - burn fuses
 - AB'
 - A'B
 - OR
 - all other gates are unused
- can implement 6 XORs
 - 12 in, 6 out, 12 AND, 6 OR
 - 50-12=38 AND gates unused



Lubomir Bic

22

Shifters

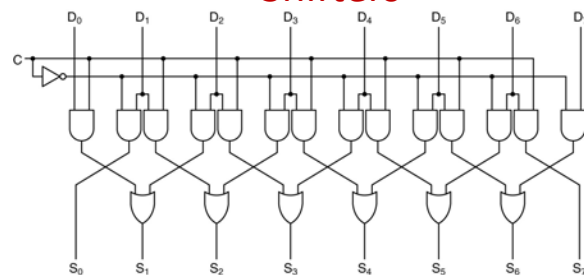


- interface
 - n inputs
 - n outputs
 - 1 control line
- basic idea:
 - if C=0, shift all inputs left by one bit
 - if C=1, shift right

Lubomir Bic

23

Shifters

 

- how does it work?
 - each D_i is connected to 2 AND gates
 - C determines which gate is opened
 - E.g., C=1 then every D_i goes to S_{i+1}
 - Note: shift is not circular, outer-most bit is lost
 - E.g., C=1 then $S_0=0$ and D_7 is lost

Lubomir Bic


24

Adders

A Half Adder

- adding 2 bits produces a sum bit and a carry bit

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

- carry propagates to the next higher-order bit
- to add multi-bit numbers need circuit with input carry


Lubomir Bic

25

Adders

A Full Adder

A	B	C _{in}	Sum	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


- Sum=1 if odd number of A, B, C_{in} are 1 (2 XOR gates)
- C_{out}=1 if A, B, C_{in} add up to more than 1, i.e.:
 - when AB=11, regardless of C_{in} (first AND gate), or
 - one of A or B is 1 (given by first XOR) and C_{in}=1 (second AND)

Lubomir Bic

26

Adders

 - A multi-bit adder simply replicates n Full Adders
 - a Ripple Carry Adder



Lubomir Bic

27

Arithmetic Logic Units

- An ALU combines multiple operations

- 1-bit ALU

- inputs:

- A, B, F, C_{in}

- assume

- ENA=ENB=1
- INVA=0
- A, B go to LU, FU

- Logical Unit:


- AB, A+B, B'

- selected by F

- e.g. F=00

- with F=11:

- adder enabled

 


Lubomir Bic

28

Arithmetic Logic Units

 - n-bit ALU is constructed from n 1-bit ALUs
- each 1-bit ALU is a “bit slice”



- depending on F, performs:
 - AB, A+B, B', A+B on 8-bit numbers A and B
 - with INC=1 can increment, e.g. A+1, B+1, A+B+1

Lubomir Bic

29

Memory


- **combinational** circuits – discussed thus far
 - output depends **only on current** inputs
- **memory** circuits
 - output depends on **current and past** inputs
- memory is essential for any computer
 - holds data and instructions while manipulated by combinational circuits
- memory types:
 - latches, flip-flops, registers, RAM

Lubomir Bic

30

Latches

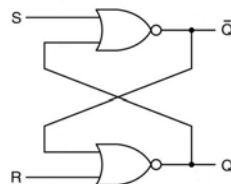- SR latch: simplest 1-bit memory circuit
- 2 inputs (S,R), 2 outputs (Q, Q')
- outputs depend on inputs **and** outputs
 - Q and Q' are complements




Lubomir Bic

31

Latches

 - basic idea:
 - 2 stable states
 - with S=R=0, Q can be 0 or 1
 - S=1 sets the latch (Q=1)
 - no change if already set
 - R=1 resets (Q=0)
 - no change if already reset




Lubomir Bic

32

Latches

 - what happens when $S=R=1$?
 - $Q=Q'=0$
 - but when $S=R=0$ again, new state is **nondeterministic**
 - solution: D latch




- Clock signal
 - permits set/reset only during a specific interval (strobe)

Lubomir Bic

33

Flip-Flops

 - what happens when D keeps changing while clock=1?
- better: capture D at a precise instant of time
 - need a circuit to generate a short pulse
 - flip-flop captures D at that moment:
 - flip-flop: **edge-triggered** vs. latch: **level-triggered**




- how does the pulse-generating circuit work?

Lubomir Bic

34

Flip-Flops

- pulse-generating circuit

 


Lubomir Bic

35

Registers

 - combine flip-flops on a chip:
- 8-bit register
 - outputs:
 - $Q_i=2,4,6,8,13,15,17,19$
 - an 8-bit number currently stored
- inputs:
 - $D_i=3,5,7,9,12,14,16,18$
 - clock (CK)=pin 11
 - clear (CLR)=pin 1



Lubomir Bic

36

RAM Memory


- RAM: random access memory
 - a block of n-bit **words** (rows of n bits)
 - need **address** to select word
 - can **read or write**
- interface
 - n input bits I_i (one n-bit word to be written)
 - n output bits O_i (one n-bit word to be read)
 - k address lines (to select among 2^k words)
 - RD/WR control
 - additional chip controls

Lubomir Bic

37

4x3 RAM

 - CS: chip select
- OE: output enable
- A: 2-bit address:
decoded to 4 rows
Ex: A=01
- RD=1: read
 $Q_i \rightarrow O_i$
- RD=0: write
 $I_i \rightarrow D_i$




Lubomir Bic

38

Computer Buses

 - a bus is a **pathway** (parallel wires) between devices
 - can be **internal** to CPU: ALU to registers
 - external to CPU: connect to memory or I/O devices
- master**: initiate transfer
- slave**: respond to request



Lubomir Bic, UCI

39


Bus Clocking

- synchronous** bus
 - driven by clock
 - square wave with frequency 5 MHz – 100 MHz
 - 1 MHz = 1 million cycles/sec
 - Example: 100 MHz $\rightarrow 10^8$ cycles/ 10^9 ns $\rightarrow$ 1 cycle = 10 ns
- assume a **memory** bus and a **read** operation
 - CPU places memory address on address lines
 - CPU commands memory to read
 - memory places content on data lines
 - CPU copies data and informs memory

Lubomir Bic, UCI

40

Bus Clocking

 


operations need to obey mutual **timing constraints**

- T_{AD} : max time for CPU to output address
- T_{ML} : min time for CPU to wait before MREQ (mem spec)
- T_M/T_{RL} : max time for CPU to request operation
- T_{DS} : min time for memory to output data
- T_{MH}/T_{RH} : max time for CPU to signal that it copied data

Lubomir Bic, UCI

41

Bus Clocking

 

Q: how much time does memory have to produce data?

$$\text{A1: } 15 - T_{AD} - T_{DS} = 15 - 4 - 2 = 9 \text{ ns}$$

$$\text{A2: } 10 - T_M - T_{DS} = 10 - 3 - 2 = 5 \text{ ns}$$


- A1 is NOT subsumed by A2 because T_{ML} could be negative
- i.e., MREQ and RD could be asserted before address is stable
- However, T_{ML} must be positive for **write** operation (address must be stable before operation is invoked)

Lubomir Bic, UCI

42

Bus Clocking

 - now assume memory needs 13 ns to produce data
- memory inserts **wait cycle**
- now it has up to 15 ns to produce data (using constraint A2)



Lubomir Bic, UCI

43

Bus Clocking


- drawbacks of synchronous buses
 - all operations must be in **multiples** of clock cycles
 - see previous example: memory has 15ns; if it needs 16ns, entire read cycle expands by 10ns (additional clock period)
 - cannot take advantage of future faster memory
- **asynchronous** bus
 - no master clock
 - bus cycle can be any length and can vary for any device
 - CPU and device use **handshake** protocol to request operation and signal availability of data

Lubomir Bic, UCI

44

Bus Clocking

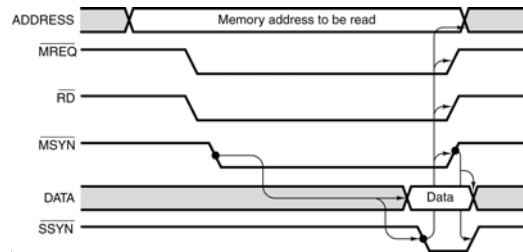- CPU places memory address on address lines
- CPU commands memory to read (MREQ, RD)
- CPU asserts MSYN (master synchronization signal)
- memory places content on data lines asap
- memory asserts SSYN (slave synchronization signal)
- CPU copies data and negates MSYN (and all other lines)
- memory negates SSYN (completing the cycle)



Block Transfers

- reading/writing one word at a time is inefficient (needs several clock cycles)
- when an entire block is needed (e.g. when caching) the bus may support block transfer operations

